

CS1011: 數位電子導論

Filters

Outline

- ▣ Introduction
- ▣ High-pass/Low-pass Filter Examples
- ▣ RC Filters
- ▣ RL Filters
- ▣ Band-pass Filter
- ▣ Band-stop Filter
- ▣ LC Oscillator
- ▣ RLC Circuit

Introduction


- It is sometimes desirable to have circuits capable of selectively filtering one frequency or range of frequencies out of a mix of different frequencies in a circuit
 - ◆ A common need for filter circuits is in high-performance stereo systems, where certain ranges of audio frequencies need to be amplified or suppressed for best sound quality and power efficiency
- A circuit designed to perform this frequency selection is called a *filter*
- Two important behaviors in the capacitor and inductor
 - ◆ The voltage across a capacitor cannot change instantaneously, since

$$V = \frac{Q}{C} = \frac{1}{C} \int I dt$$

- ◆ The current through an inductor cannot change instantaneously, since


$$V = L \frac{dI}{dt}$$

High-pass Filter Example

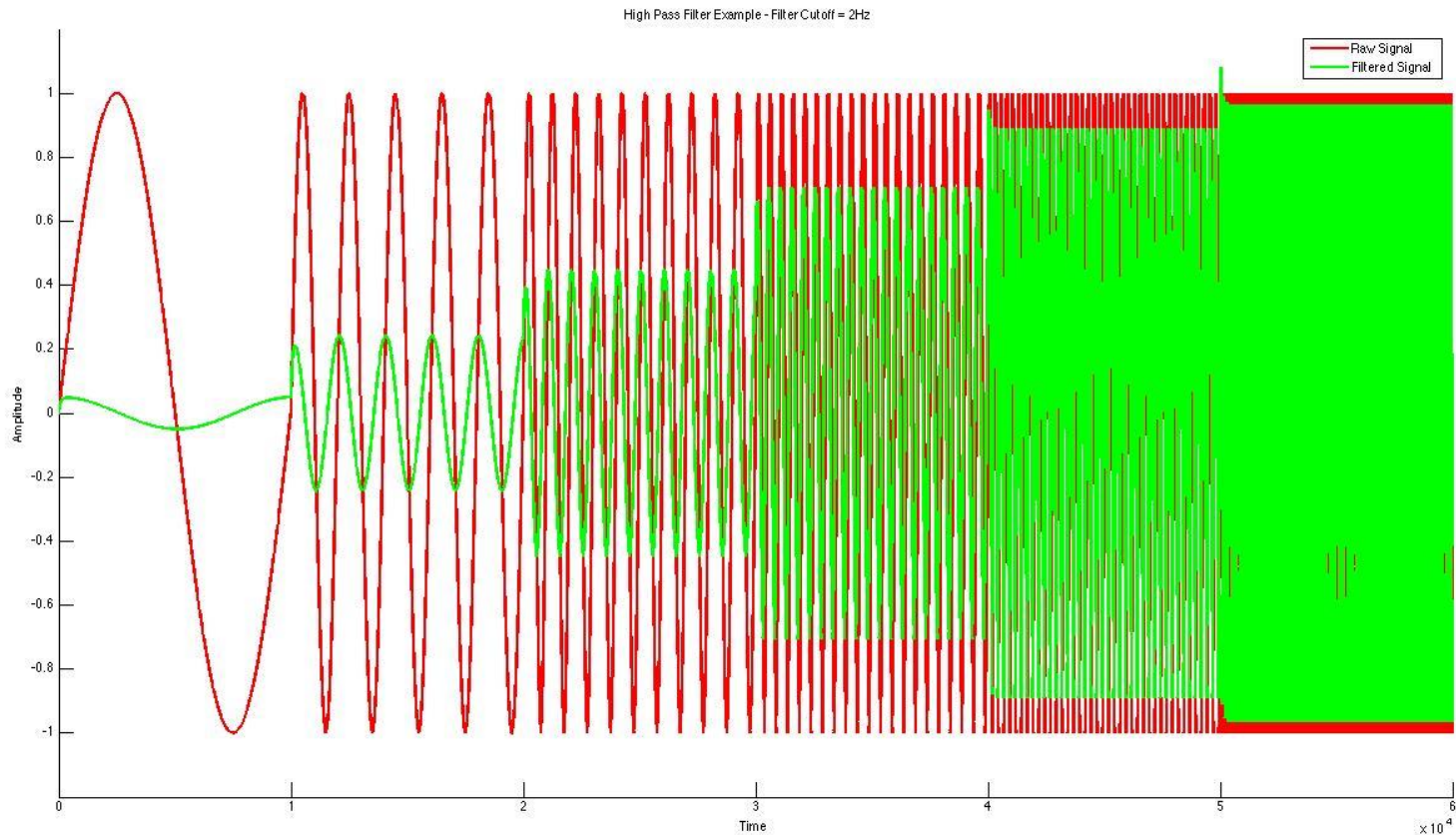

<http://www.nickgillian.com/wiki/pmwiki.php/GRT/HighPassFilter>

Low-pass Filter Example

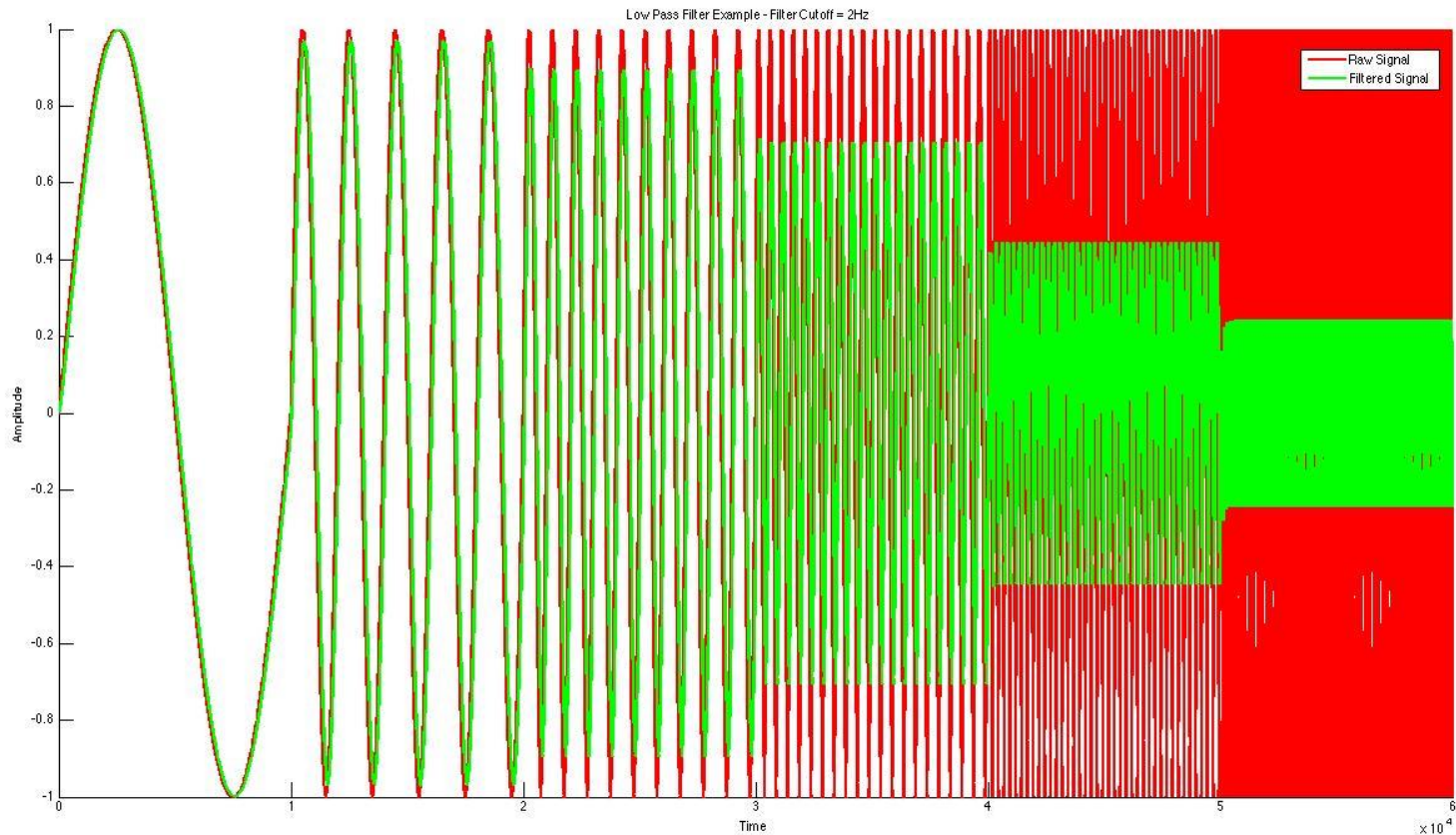


<http://www.nickgillian.com/wiki/pmwiki.php/GRT/LowPassFilter>


High-pass (Low-cut) RC Filter

■ Consider the following circuit

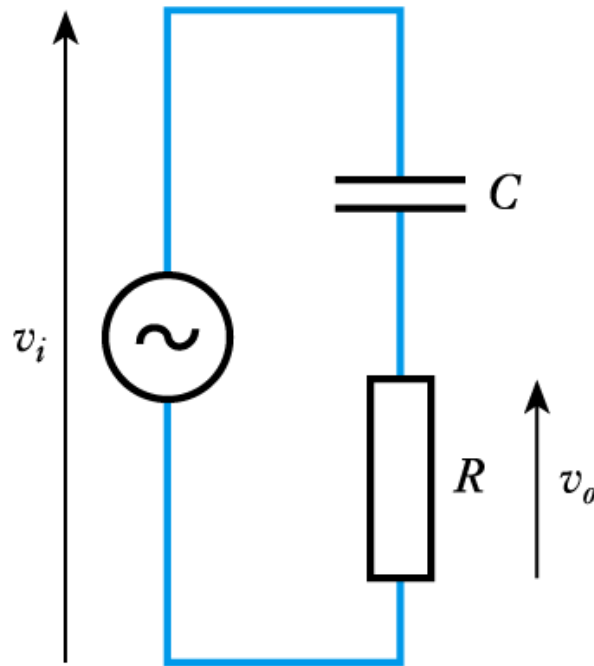- ◆ Capacitors are widely used in electronic circuits for blocking direct current (low-cut) while allowing alternating current to pass (high-pass)




(a)

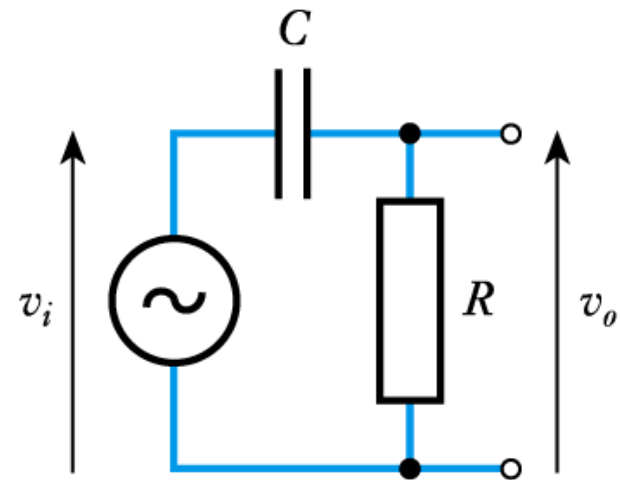

(b)


Low-pass (High-cut) RC Filter

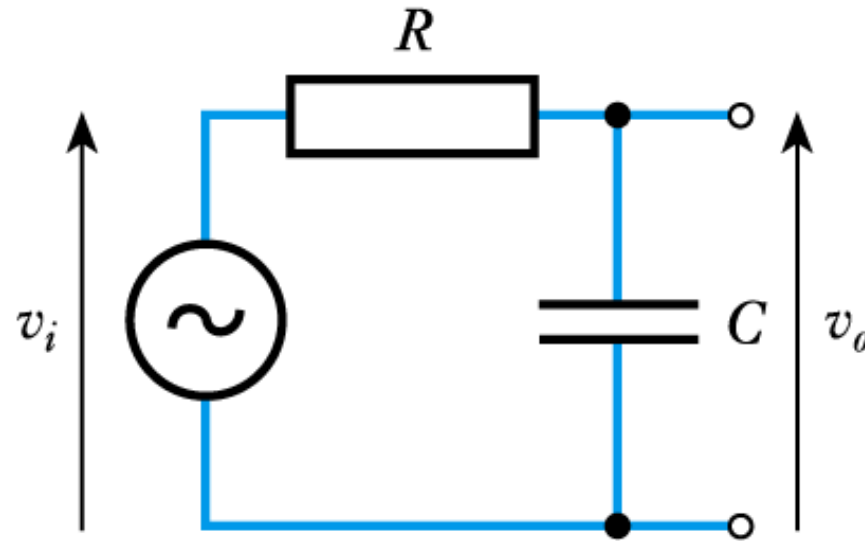- Transposing the C and R gives a very different behavior




Low-pass (High-cut) RL Filter

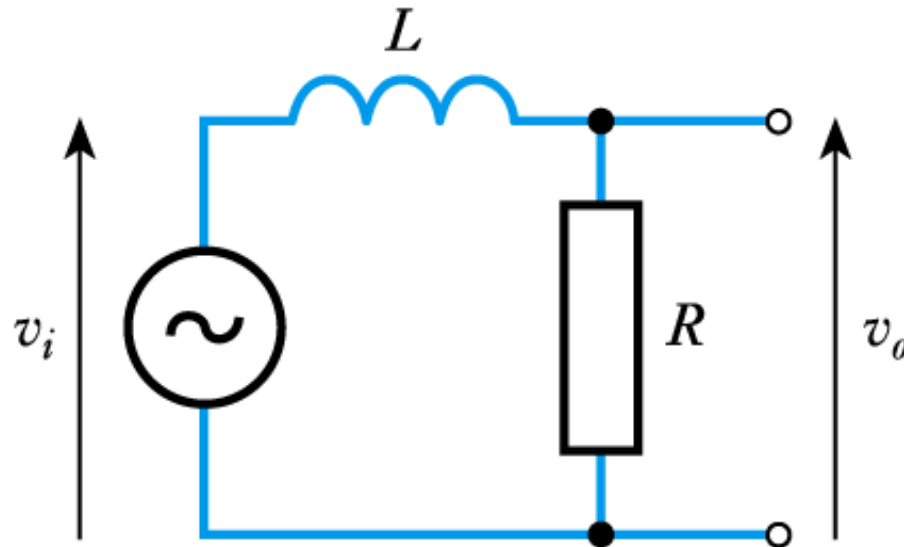- Low-pass networks can also be produced using *RL* circuits
 - ◆ Inductors are widely used in alternating current electronic equipment for blocking AC (high-cut) while allowing DC to pass (low-pass)




High-pass (Low-cut) RL Filter

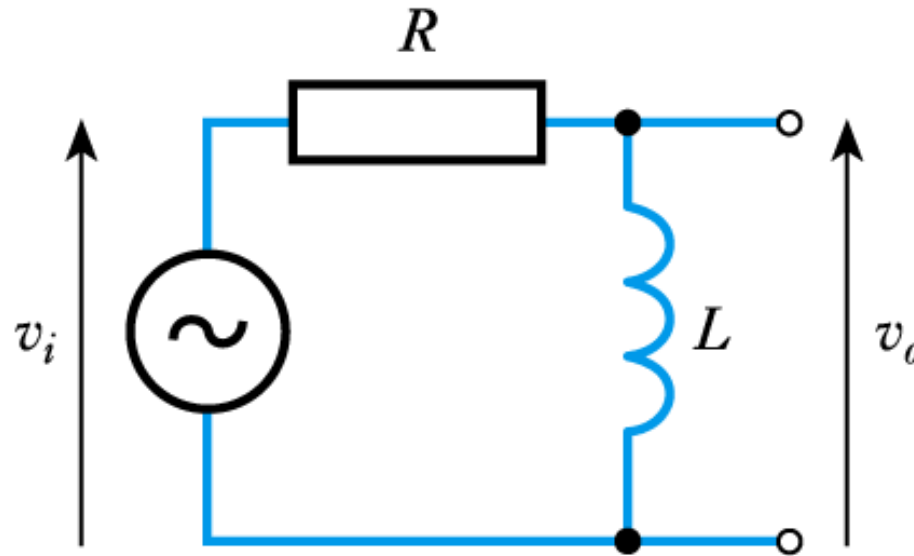- Transposing the L and R gives a very different behavior





Band-pass Filter

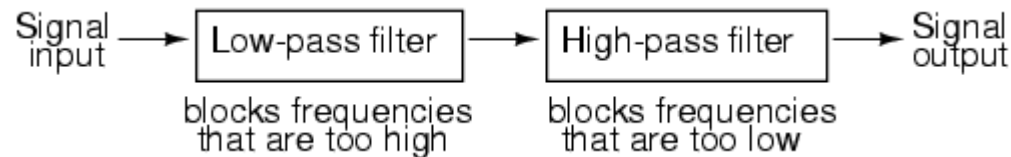■ System level block diagram of a band-pass filter




■ Filter examples

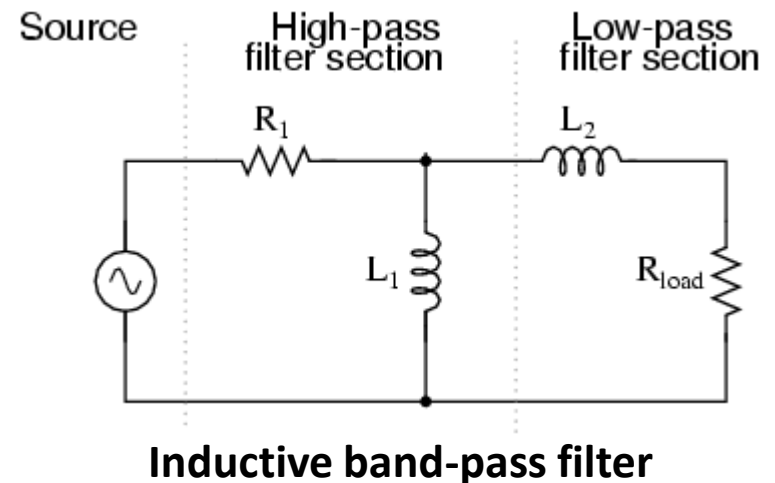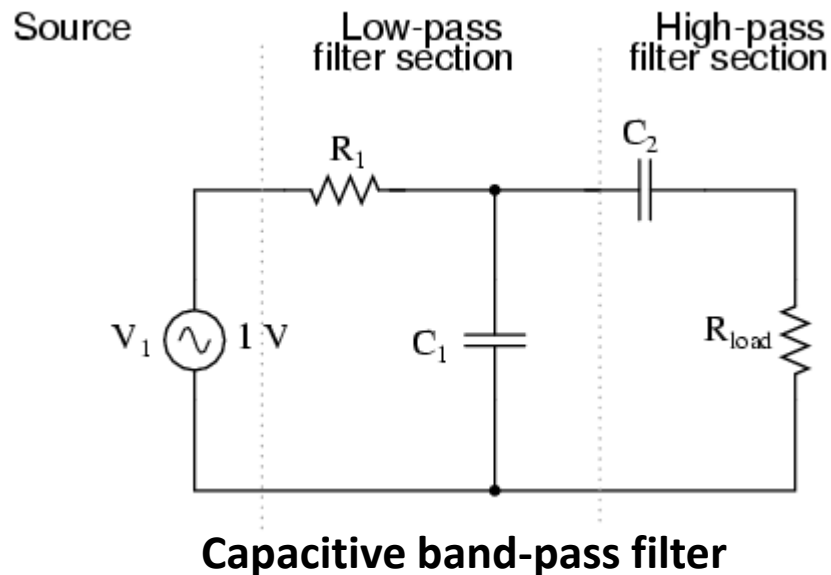


Band-stop Filter

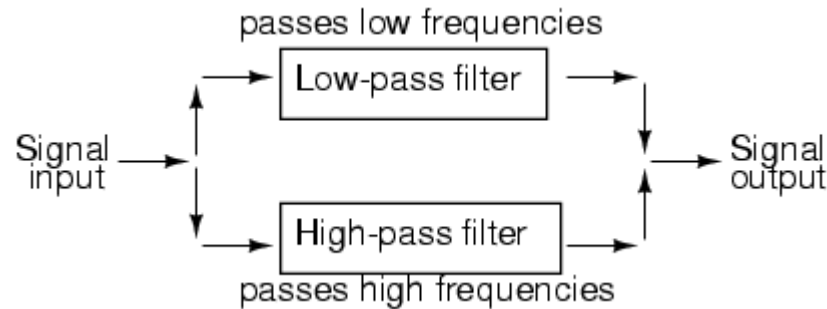■ System level block diagram of a band-stop filter



■ Filter example

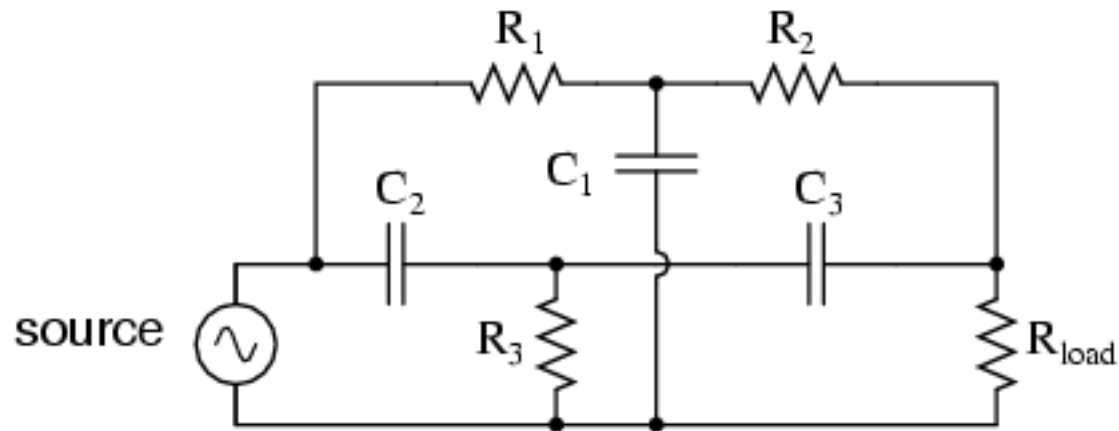

“Twin-T” band-stop filter

LC Oscillator

■ Applying Kirchhoff's voltage law

$$v_C + v_L = 0$$

■ (a) in a capacitor (b) in an inductor

$$i = C \frac{dv}{dt}$$


$$v_L = L \frac{di}{dt}$$

■ Which substituting gives

$$v + LC \frac{d^2v}{dt^2} = 0$$

■ Solve the differential equation

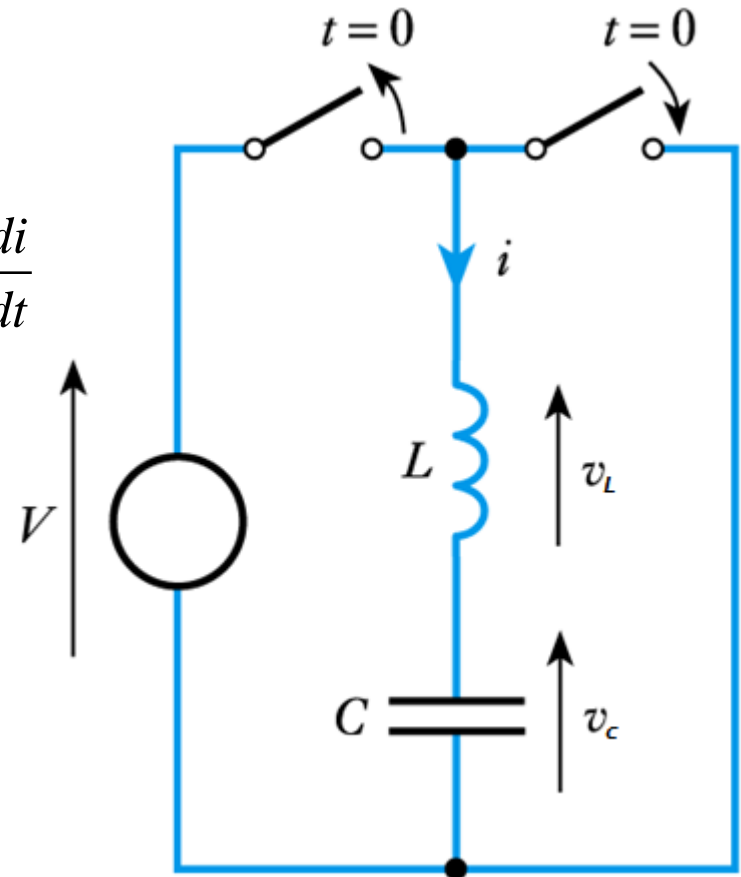- ◆ 1. Guess a general solution
- ◆ 2. Apply the solution
- ◆ 3. Substitute by boundary condition
- ◆ 4. Verify



LC Oscillator

1. Guess a general solution

$$v(t) = \alpha \cdot \sin(\omega t + \phi) + \gamma$$

2. Apply the solution

$$v + LC \frac{d^2 v}{dt^2} = 0 \rightarrow \alpha \cdot \sin(\omega t + \phi) + \gamma - \alpha \omega^2 LC \cdot \sin(\omega t + \phi) = 0$$

$$\rightarrow \begin{cases} \alpha \cdot \sin(\omega t + \phi) - \alpha \omega^2 LC \cdot \sin(\omega t + \phi) = 0 \rightarrow \omega = \frac{1}{\sqrt{LC}} \\ \gamma = 0 \end{cases}$$


$$\therefore v(t) = \alpha \cdot \sin\left(\frac{t}{\sqrt{LC}} + \phi\right)$$





3. Substitute by boundary condition

When $t = 0, v = V, i = 0$:

$$\begin{cases} v(t=0) = \alpha \sin \phi = V \\ i(t=0) = C \frac{dv}{dt} = C \cdot \alpha \omega \cos(\phi) = 0 \end{cases} \rightarrow \phi = \frac{\pi}{2}, \alpha = V \text{ or } \phi = -\frac{\pi}{2}, \alpha = -V$$

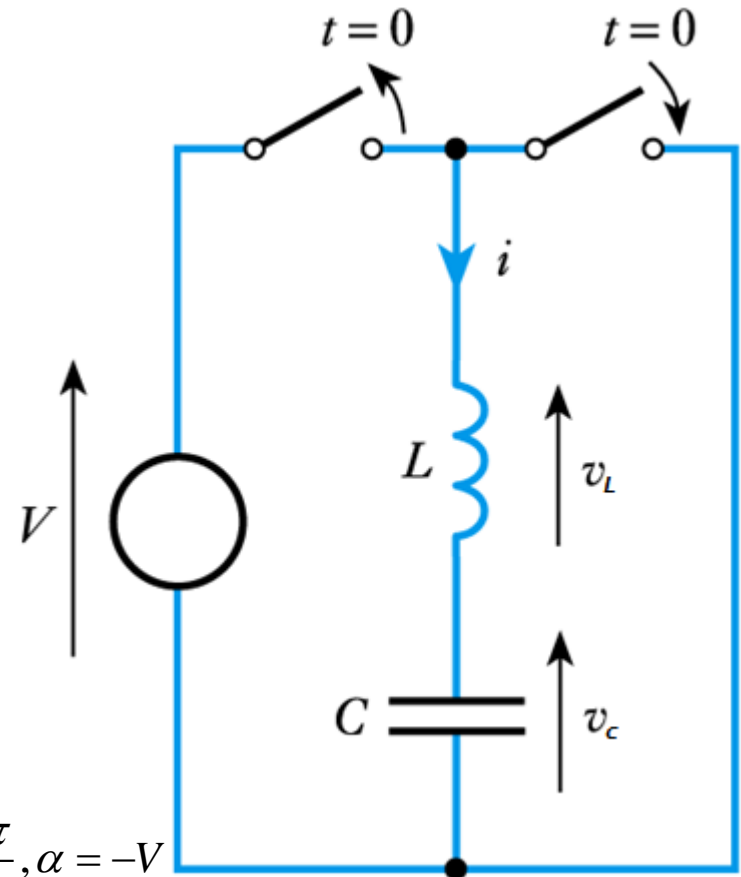
$$\therefore v(t) = V \sin\left(\frac{t}{\sqrt{LC}} + \frac{\pi}{2}\right) = V \cos \frac{t}{\sqrt{LC}}$$



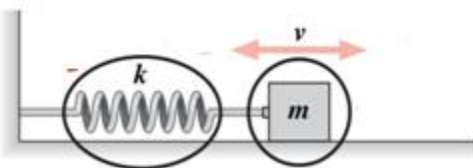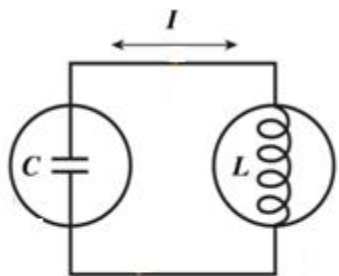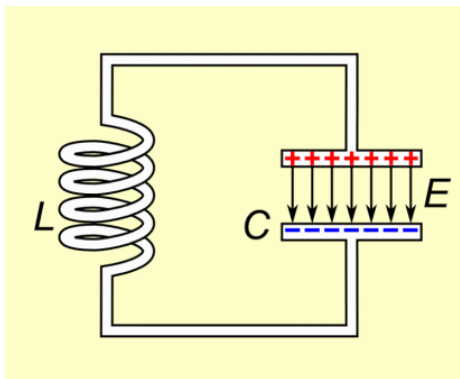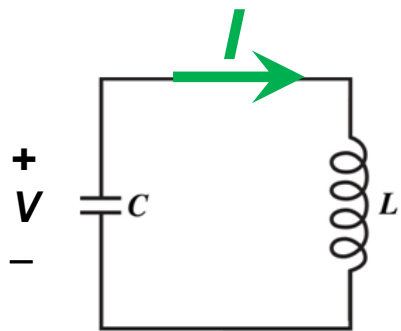

全是磁能，
在電感器內


Energy all
magnetic,
in inductor.

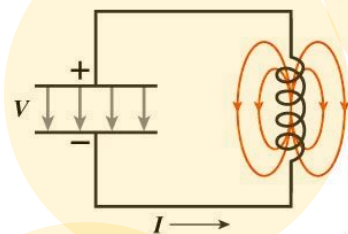

Energy all electric,
in capacitor.

全是電能，
在電容器內

(h)

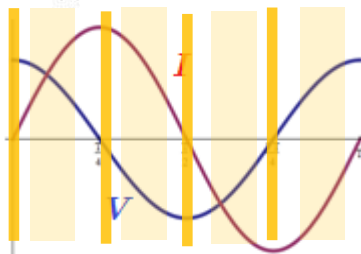

(f)

(a)

(b)

(c)

(d)

(e)

全是磁能，
在電感器內

Energy all
magnetic,
in inductor.

Energy all electric,
in capacitor.

全是電能，
在電容器內

RLC Circuit (Series Style)

- Applying Kirchhoff's voltage law

$$v_R + v_C + v_L = 0$$

- (a) in a capacitor (b) in an inductor

$$i = C \frac{dv}{dt}$$


$$v_L = L \frac{di}{dt}$$

- Which substituting gives

$$RC \frac{dv}{dt} + v + LC \frac{d^2v}{dt^2} = 0$$

- General 2-order differential equation


- ◆ Let's skip the mathematics

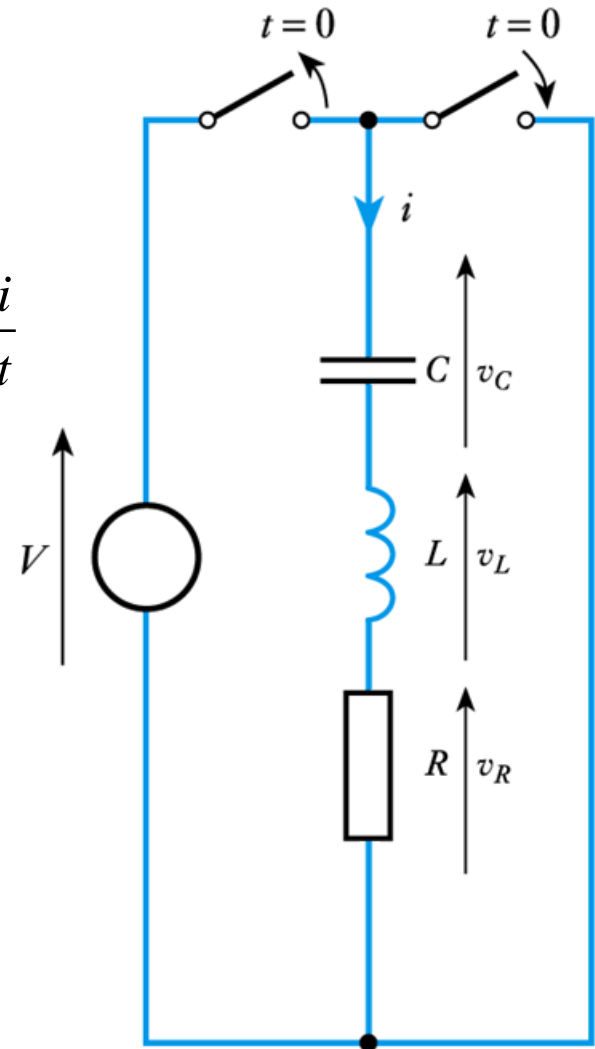




RLC Circuit (Series Style)

■ **Damping factor:** $\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$

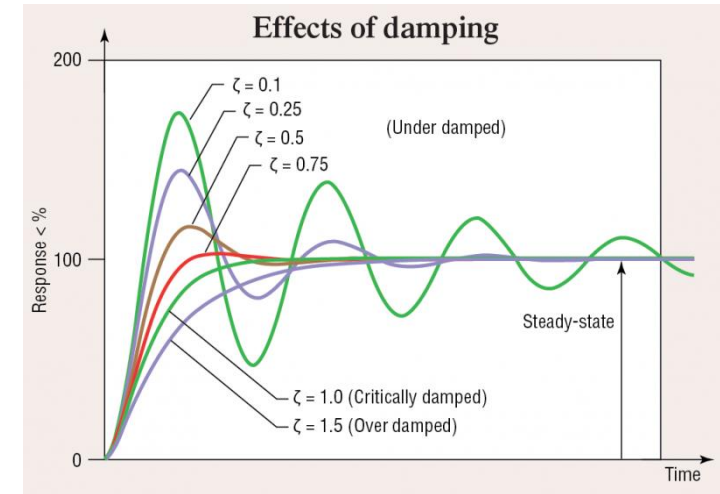- ◆ $\zeta < 1$: under damp
- ◆ $\zeta = 1$: critical damp
- ◆ $\zeta > 1$: over damp



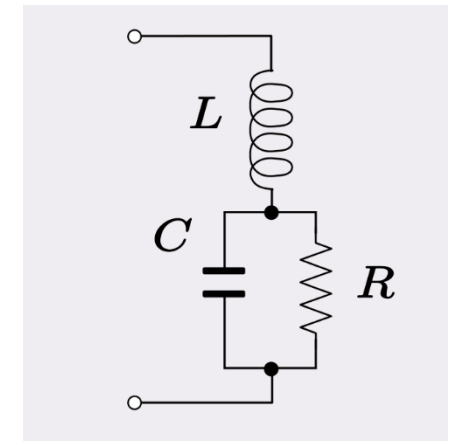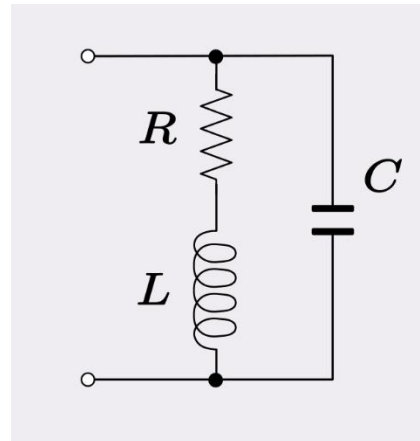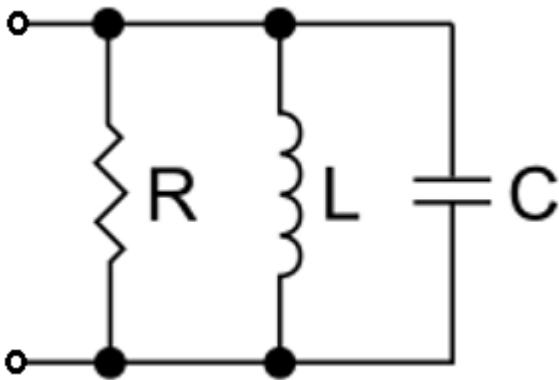■ **Miscellaneous RLC circuits for various applications**






http://www.wikiwand.com/en/RLC_circuit

RLC Circuit Resonance (Series Style)

- Given an alternating voltage source, the voltage response of the RLC circuit could oscillate

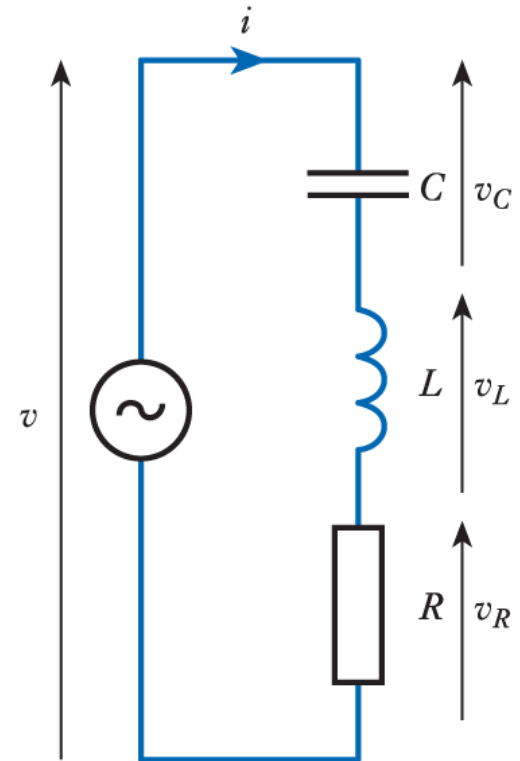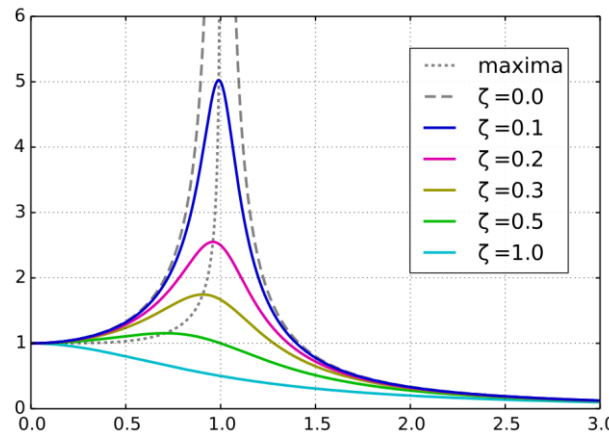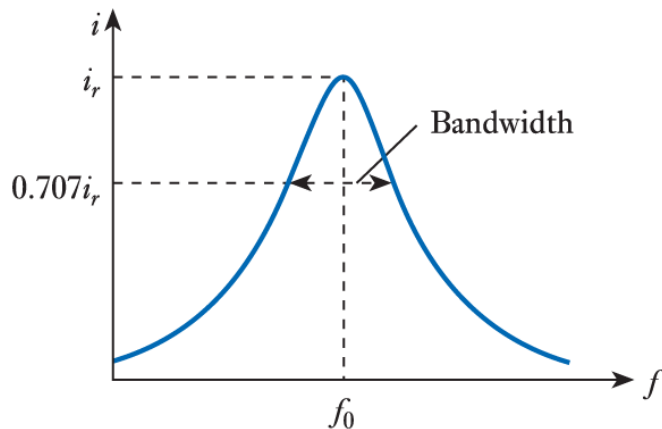◆ Resonance frequency: $\omega_o = \frac{1}{\sqrt{LC}}$, $f_o = \frac{1}{2\pi\sqrt{LC}}$



Analogies Between Electrical and Mechanical Systems

Electric Circuit		One-Dimensional Mechanical System
Charge	$Q \leftrightarrow x$	Position
Current	$I \leftrightarrow v_x$	Velocity
Potential difference	$\Delta V \leftrightarrow F_x$	Force
Resistance	$R \leftrightarrow b$	Viscous damping coefficient
Capacitance	$C \leftrightarrow 1/k$	(k = spring constant)
Inductance	$L \leftrightarrow m$	Mass
Current = time derivative of charge	$I = \frac{dQ}{dt} \leftrightarrow v_x = \frac{dx}{dt}$	Velocity = time derivative of position
Rate of change of current = second time derivative of charge	$\frac{dI}{dt} = \frac{d^2Q}{dt^2} \leftrightarrow a_x = \frac{dv_x}{dt} = \frac{d^2x}{dt^2}$	Acceleration = second time derivative of position
Energy in inductor	$U_L = \frac{1}{2} LI^2 \leftrightarrow K = \frac{1}{2} mv^2$	Kinetic energy of moving object
Energy in capacitor	$U_C = \frac{1}{2} \frac{Q^2}{C} \leftrightarrow U = \frac{1}{2} kx^2$	Potential energy stored in a spring
Rate of energy loss due to resistance	$I^2 R \leftrightarrow bv^2$	Rate of energy loss due to friction
RLC circuit	$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \leftrightarrow m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = 0$	Damped object on a spring

Key Points

- Passive circuit elements, R , L and C , can be combined in a number of different topologies, with practical importance in real circuits
- Filter is a circuit capable of selectively filtering one frequency or range of frequencies out of a mix of different frequencies
- The behavior of LC and RLC circuits are described by second-order differential equations in circuit analysis
- The resonance effect of the LC circuit has many important applications in signal processing and communications systems
- RLC circuits can be used as a band-pass filter, band-stop filter, low-pass filter or high-pass filter, based on the configurations