

CS1011: 數位電子導論

Capacitance

Outline


- ▣ Introduction
- ▣ Capacitors and Capacitance
- ▣ Alternating Voltages and Currents
- ▣ Capacitors in Series and Parallel
- ▣ Voltage and Current
- ▣ Energy Stored in a Charged Capacitor
- ▣ Circuit Symbols

Introduction


- We noted earlier that an electric current represents a flow of charge
- A capacitor can store electric charge and can therefore store electrical energy
- Capacitors are often used in association with alternating currents and voltages
- Capacitor is a key component in almost all electronic circuits

Capacitors and Capacitance

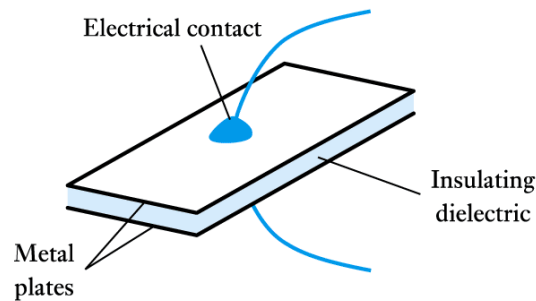
- Capacitors consist of two conducting surfaces separated by an insulating layer called a **dielectric**



(a) A parallel-plate capacitor

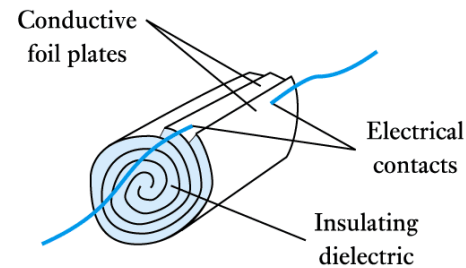

(b) A cylindrical capacitor

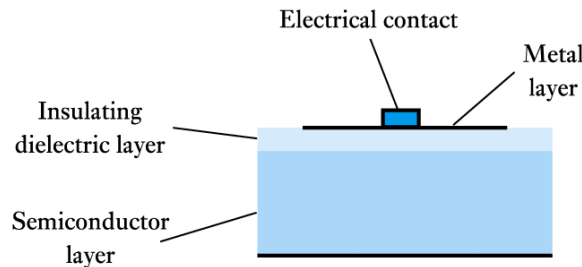

(c) An integrated circuit capacitor

- Supercapacitors are widely used in transportation and energy harvesting applications



Energy Storage Technology Comparisons

Parameter	Aluminum Electrolytic Capacitor	Double-layer Capacitor	Pseudocapacitor	Hybrid (Li-ion)	Lithium-ion Battery
Temperature Range	-40 ~ +125 °C	-40 ~ +70 °C	-20 ~ +70 °C	-20 ~ +70 °C	-20 ~ +60 °C
Maximum Voltage	4 ~ 630 V	1.2 ~ 3.3 V	2.2 ~ 3.3 V	2.2 ~ 3.8 V	2.5 ~ 4.2 V
Recharge Cycles	< unlimited	100 k ~ 1 000 k	100 k ~ 1 000 k	20 k ~ 100 k	0.5 k ~ 10 k
Capacitance	≤ 2.7 F	0.1 ... 470 F	100 ... 12 000 F	300 ... 3 300 F	—
Energy Density	0.01 ~ 0.3 Wh/kg	1.5 ~ 3.9 Wh/kg	4 ~ 9 Wh/kg	10 ~ 15 Wh/kg	100 ~ 265 Wh/kg
Power Density	> 100 W/g	2 ~ 10 W/g	3 ~ 10 W/g	3 ~ 14 W/g	0.3 ~ 1.5 W/g
Self-discharge	short (days)	Medium (weeks)	Medium (weeks)	Long (months)	Long (months)
Efficiency (%)	99%	95%	95%	90%	90%
Working Life	> 20 years	5 ~ 10 years	5 ~ 10 years	5 ~ 10 years	3 ~ 5 years

Wikipedia: <https://en.wikipedia.org/wiki/Supercapacitor>

A Simple Capacitor Circuit

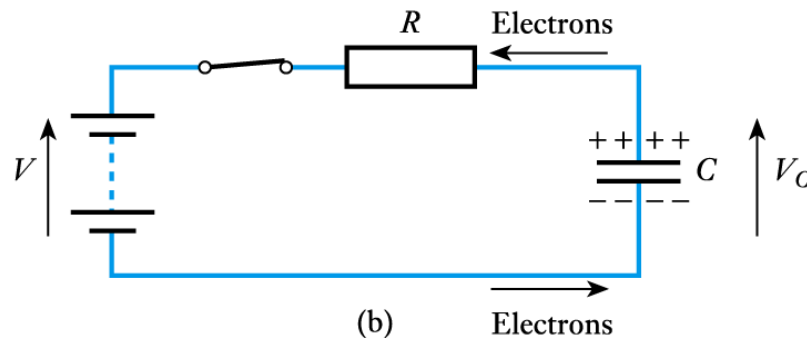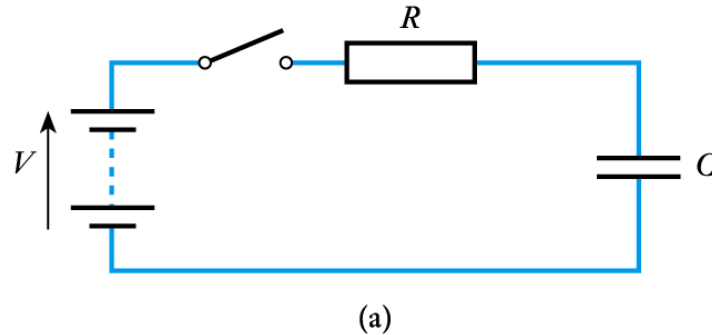- When switch is closed, electrons flow from top plate into battery and from battery onto bottom plate
- Charge produces an electric field across the capacitor and a voltage across it



Capacitance Property

- For a given capacitor, the **stored charge q** is directly proportional to the voltage V across it
- The constant of proportionality is the **capacitance C** and thus

$$C = \frac{Q}{V}$$

- If the charge is measured in **coulombs** and the voltage in **volts**, then the capacitance is in **farads**

Example

- A 10 μF capacitor has 10 V across it. What quantity of charge is stored in it?

$$C = \frac{Q}{V}$$


$$Q = CV$$

$$= 10^{-5} \times 10$$

$$= 100 \mu\text{C}$$

Alternating Voltages and Currents

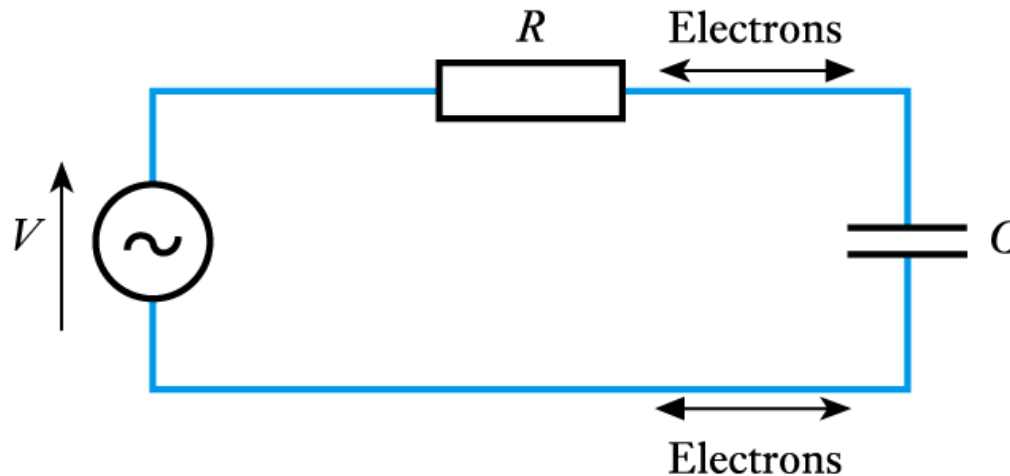
- A constant current cannot flow through a capacitor
 - ◆ However, since the voltage across a capacitor is proportional to the charge on it, an alternating voltage must correspond to an alternating charge, and hence to current flowing into and out of the capacitor
 - ◆ This can give the impression that an alternating current flows through the capacitor



A Mechanical Analogy of a Capacitor

■ A mechanical analogy may help to explain this

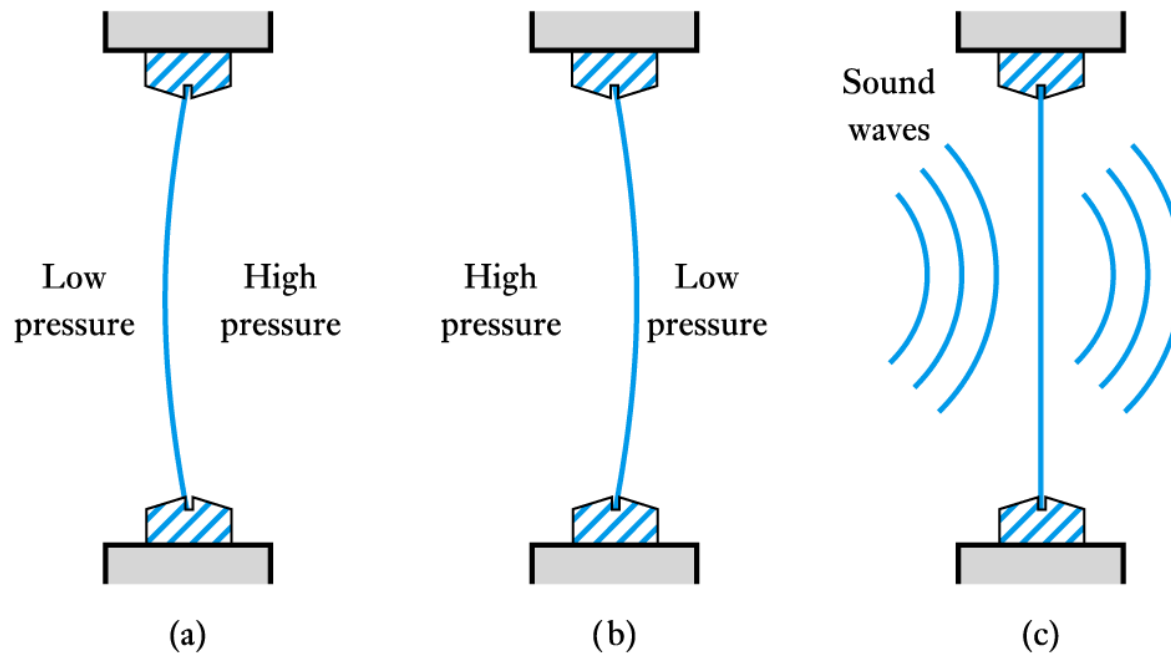- ◆ Consider a window - air cannot pass through it, but sound (which is a fluctuation in air pressure) can



Capacitors in Parallel

- Consider a voltage V applied across two capacitors
- The charge on each capacitor is

$$Q_1 = VC_1$$


$$Q_2 = VC_2$$

- If the two capacitors are replaced with a single capacitor C which has a similar effect as the pair, then

$$\text{Charge stored on } C = Q_1 + Q_2$$

$$VC = VC_1 + VC_2$$


$$C = C_1 + C_2$$

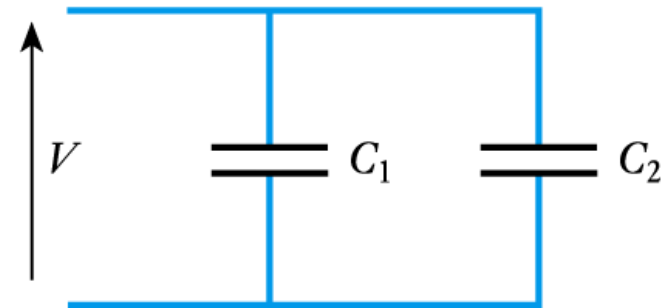

Capacitors in Series

- Consider a voltage V applied across two capacitors in series
- The only charge that can be applied to the lower plate of C_1 is that supplied by the upper plate of C_2 .
- Therefore the charge on each capacitor must be identical.
Let this be Q , and therefore if a single capacitor C has the same effect as the pair, then
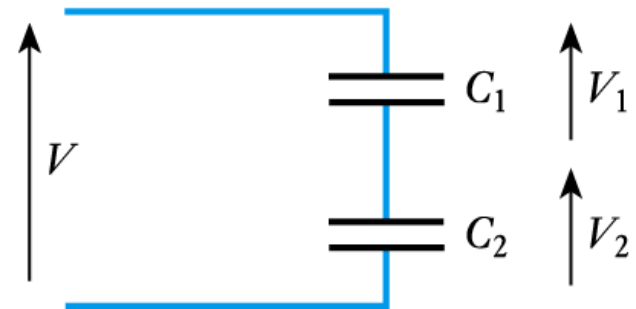
$$V = V_1 + V_2$$
$$\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2}$$
$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$



Voltage and Current

- The voltage across a capacitor is directly related to the charge on the capacitor

$$V = \frac{Q}{C} = \frac{1}{C} \int I dt$$

- Alternatively, since $Q = CV$ we can see that




$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

and since dQ/dt is equal to current, it follows that

$$I = C \frac{dV}{dt}$$

Charging Capacitors

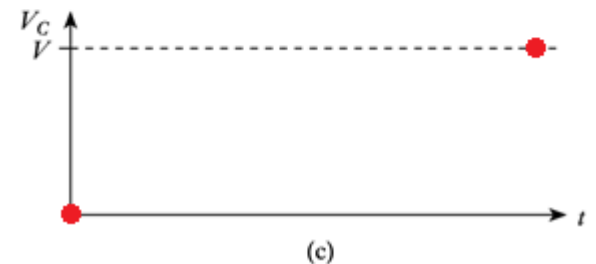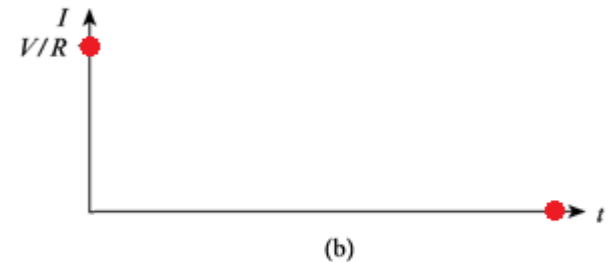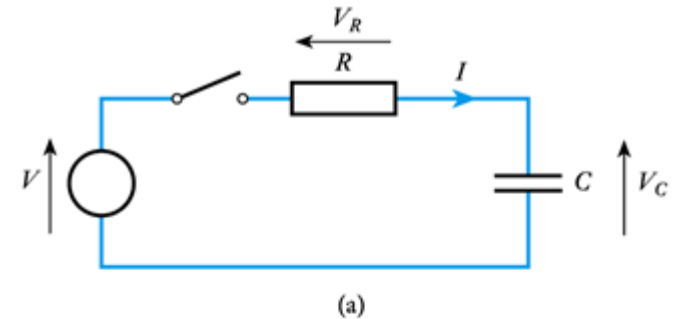- Capacitor is initially discharged
 - ◆ Voltage across it will be zero
- Switch is closed at $t = 0$
- V_C is initially zero
 - ◆ Hence, V_R is initially V
 - ◆ Hence, I is initially V/R
- As the capacitor charges...
 - ◆ V_C increases
 - ◆ V_R decreases
 - ◆ Hence, I decreases
- When the capacitor is fully charged
 - ◆ $t \rightarrow \infty$
 - ◆ $V_C = V$
 - ◆ $V_R = 0$
 - ◆ $I = 0$



Charging Capacitors

■ Applying Kirchhoff's voltage law

$$iR + v = V$$

■ Now, in a capacitor


$$i = C \frac{dv}{dt}$$

■ Which substituting gives

$$RC \frac{dv}{dt} + v = V$$

■ Solve the differential equation

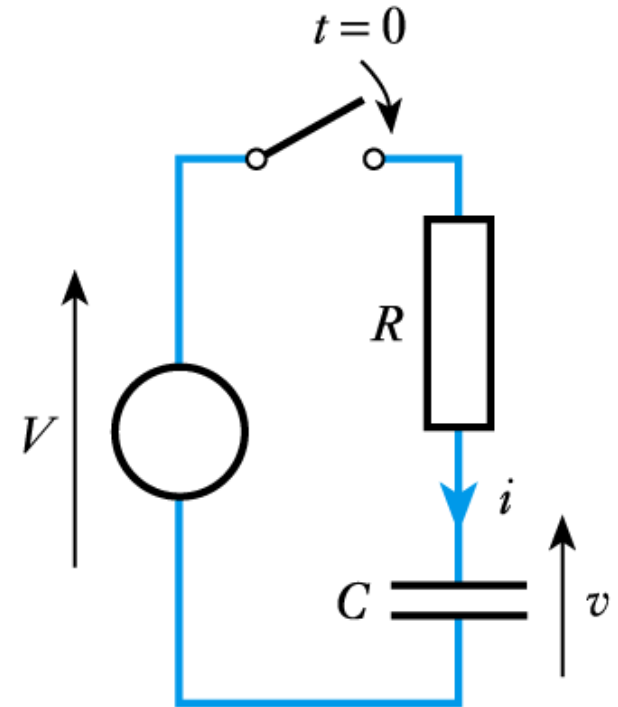- ◆ 1. Guess a general solution
- ◆ 2. Apply the solution
- ◆ 3. Substitute by boundary condition
- ◆ 4. Verify the equation



Charging Capacitors

1. Guess a general solution

$$v(t) = \alpha \cdot e^{\beta t} + \gamma$$

2. Apply the solution

$$RC \frac{dv}{dt} + v = V \rightarrow RC \cdot \alpha \beta \cdot e^{\beta t} + \alpha \cdot e^{\beta t} + \gamma = V$$

$$\rightarrow \begin{cases} RC \cdot \alpha \beta \cdot e^{\beta t} + \alpha \cdot e^{\beta t} = 0 \rightarrow \beta = -\frac{1}{RC} \\ \gamma = V \end{cases}$$


$$\therefore v(t) = \alpha \cdot e^{-\frac{t}{RC}} + V$$

3. Substitute by boundary condition

When $t = 0, v = 0$:

$$v(t) = \alpha \cdot e^{-\frac{t}{RC}} + V = \alpha + V = 0 \rightarrow \alpha = -V$$
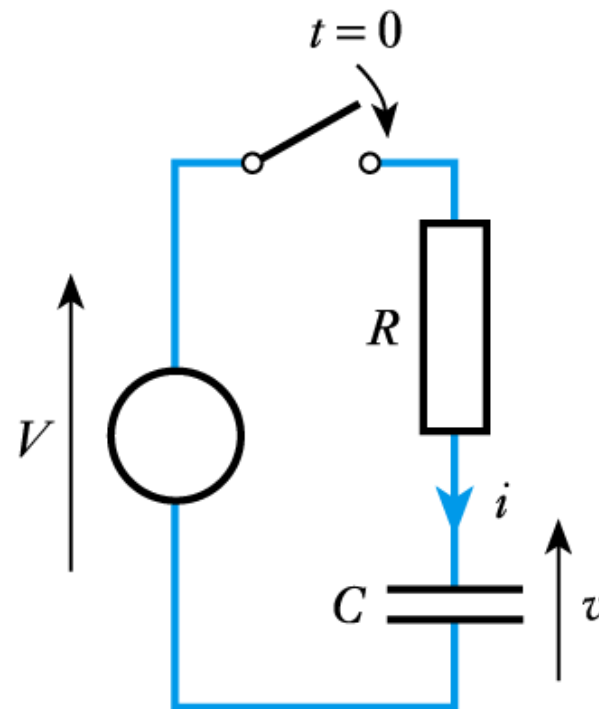
$$\therefore v(t) = -Ve^{-\frac{t}{RC}} + V = V(1 - e^{-\frac{t}{RC}})$$



Discharging Capacitors

- Applying Kirchhoff's voltage law

$$iR + v = 0$$

- Now, in a capacitor


$$i = C \frac{dv}{dt}$$

- Which substituting gives

$$RC \frac{dv}{dt} + v = 0$$

- Solve the differential equation

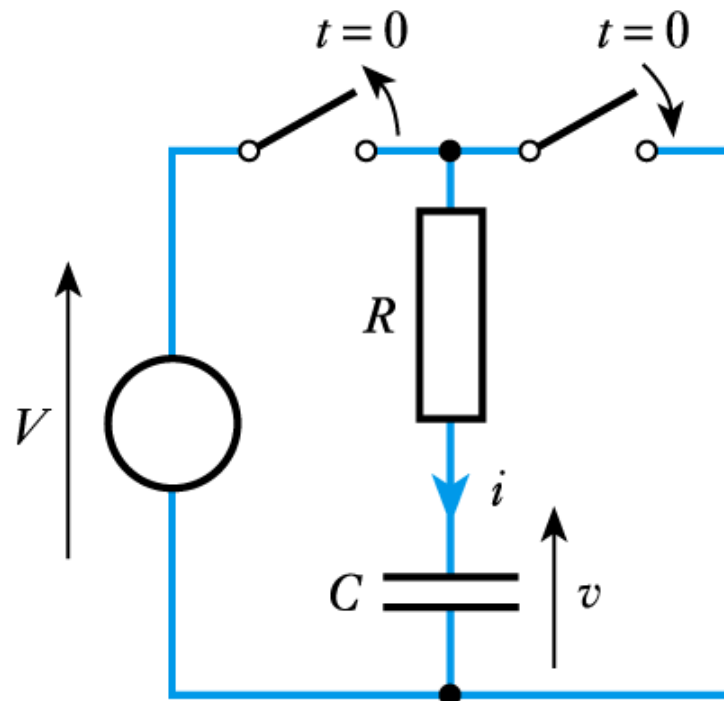- ◆ 1. Guess a general solution
- ◆ 2. Apply the solution
- ◆ 3. Substitute by boundary condition
- ◆ 4. Verify the equation



Discharging Capacitors

1. Guess a general solution

$$v(t) = \alpha \cdot e^{\beta t} + \gamma$$

2. Apply the solution

$$RC \frac{dv}{dt} + v = 0 \rightarrow RC \cdot \alpha \beta \cdot e^{\beta t} + \alpha \cdot e^{\beta t} + \gamma = 0$$

$$\rightarrow \begin{cases} RC \cdot \alpha \beta \cdot e^{\beta t} + \alpha \cdot e^{\beta t} = 0 \rightarrow \beta = -\frac{1}{RC} \\ \gamma = 0 \end{cases}$$


$$\therefore v(t) = \alpha \cdot e^{-\frac{t}{RC}}$$

3. Substitute by boundary condition


When $t = 0, v = V$:

$$v(t) = \alpha \cdot e^{-\frac{t}{RC}} = \alpha = V \rightarrow \alpha = V$$


$$\therefore v(t) = Ve^{-\frac{t}{RC}}$$

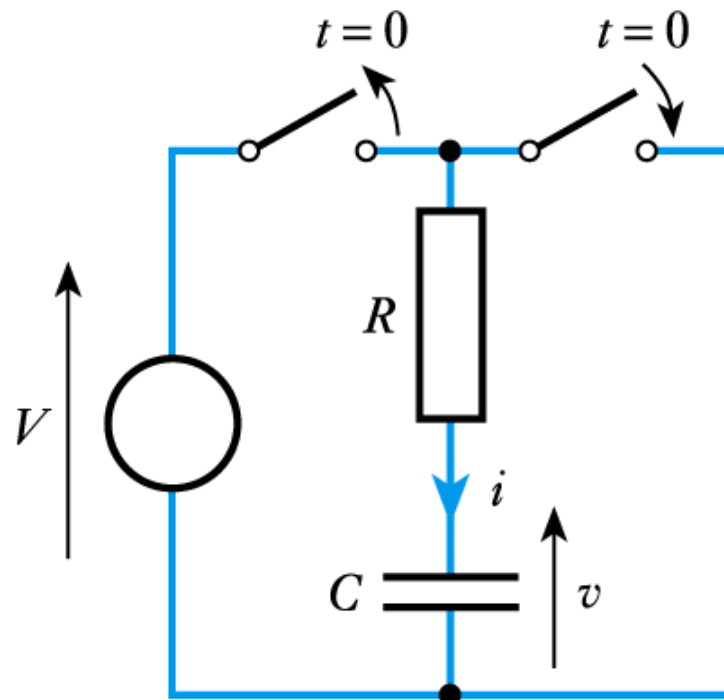

The Nature of Exponential Curves

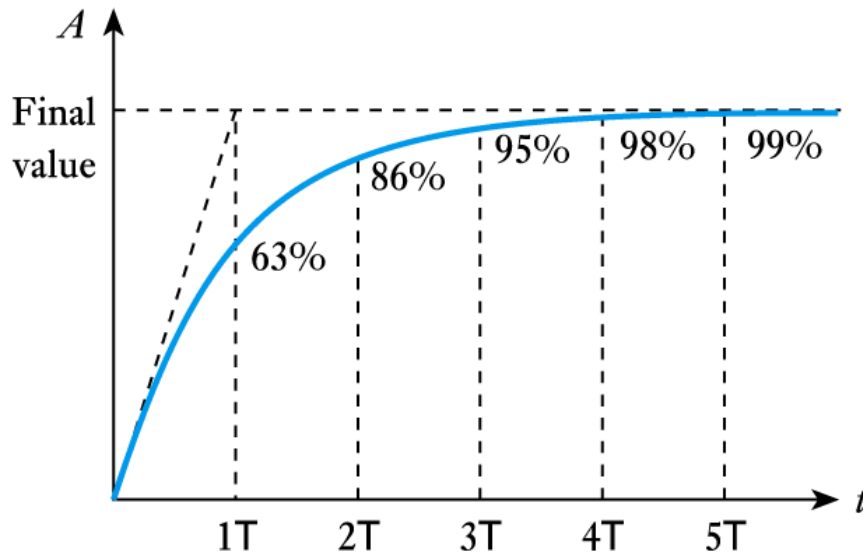

(a) $A(1 - e^{-t/T})$

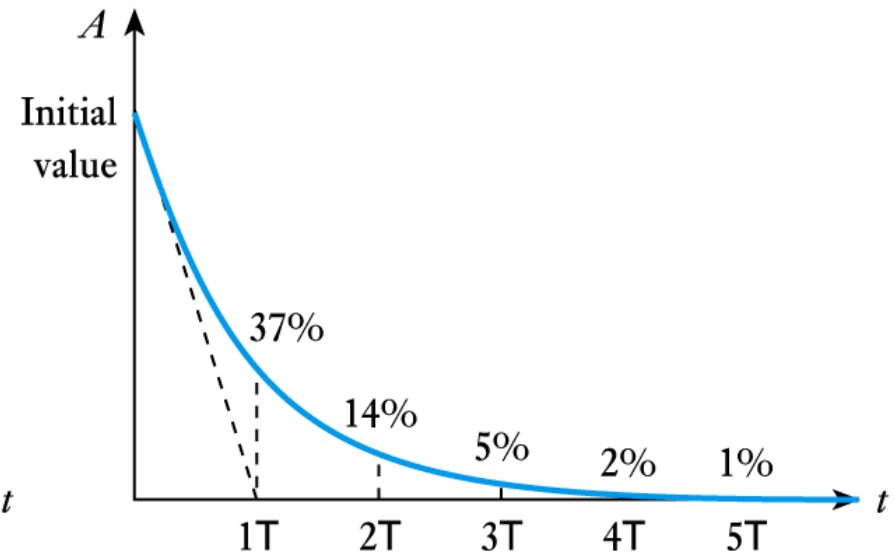

(b) $A e^{-t/T}$

Time Constant

■ Capacitor charging


$$v(t) = -Ve^{-\frac{t}{RC}} + V = V(1 - e^{-\frac{t}{RC}}) = V(1 - e^{-\frac{t}{T}})$$

■ Capacitor discharging


$$v(t) = Ve^{-\frac{t}{RC}} = Ve^{-\frac{t}{T}}$$

- Charging/discharging current is determined by R and the voltage v across it
- Increasing R will increase the time taken to charge/discharge C
- Increasing C will also increase time taken to charge/discharge C
- Time required to charge/discharge to a particular voltage is determined by the product RC
- This product is the **time constant T** (greek tau, τ)


Charging and Discharging Summary

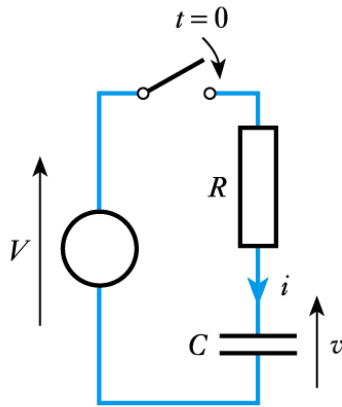


(a)

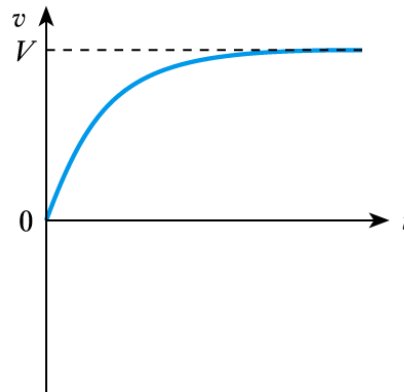


(b)

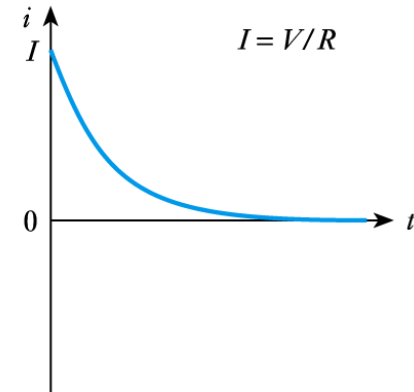


(c)

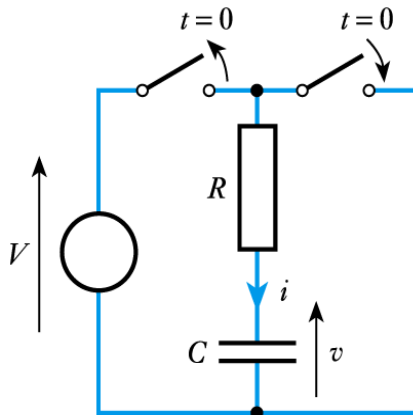

(a)

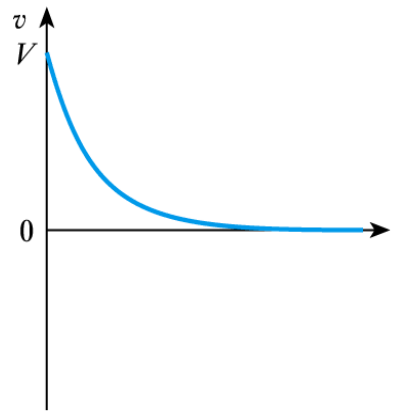

(b)

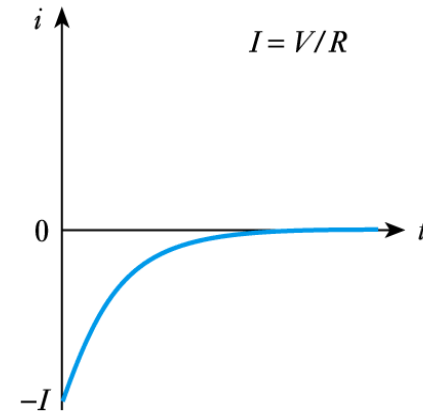

(c)

Energy Stored in a Charged Capacitor

- To move a charge Q through a potential difference ΔV requires an amount of energy $Q \Delta V$
- As we charge up a capacitor, we repeatedly add small amounts of charge ΔQ by moving them through a voltage equal to the voltage on the capacitor
- Since $Q = CV$, it follows that $\Delta Q = C \Delta V$, so the energy needed E is given by

$$E = \int_0^V CV dV = \frac{1}{2} CV^2$$

- Alternatively, since $V = Q/C$

$$E = \frac{1}{2} CV^2 = \frac{1}{2} C \left(\frac{Q}{C} \right)^2 = \frac{1}{2} \frac{Q^2}{C}$$

Example

- Calculate the energy stored in a $10\text{ }\mu\text{F}$ capacitor when it is charged to 100 V .

$$E = \frac{1}{2}CV^2 = \frac{1}{2} \times 10^{-5} \times 100^2 = 50\text{ mJ}$$


Circuit Symbols



(a) A fixed capacitor



(b) A variable capacitor

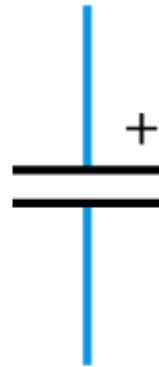

(c) A polarised capacitor



(d) A polarised capacitor

Key Points

- A capacitor consists of two plates separated by a dielectric
- The charge stored on a capacitor is proportional to V
- A capacitor blocks DC but appears to pass AC
- The capacitance of several capacitors in parallel is equal to the sum of their individual capacitances
- The capacitance of several capacitors in series is equal to the reciprocal of the sum of the reciprocals of the individual capacitances
- When a capacitor is charged through a resistor, the charging rate is determined by the time constant RC
 - ◆ Hence, the voltage across a capacitor cannot change instantaneously
- The energy stored in a capacitor is $\frac{1}{2}CV^2$ or $\frac{1}{2}Q^2/C$