

CS1011: 數位電子導論

**Basic Electric Circuits and
Components**

Outline

- Introduction
- SI Units and Common Prefixes
- Electrical Circuits
- Direct Currents and Alternating Currents
- Resistors, Capacitors and Inductors
- Ohm's and Kirchhoff's Laws
- Power Dissipation in Resistors
- Resistors in Series and Parallel
- Resistive Potential Dividers
- Sinusoidal Quantities
- Circuit Symbols

Introduction

- This lecture outlines the basics of **Electrical Circuits**
 - ◆ For most students, much of this will be familiar...?!
 - ◆ If there is any topic that you are unsure of (or that are new to you), you should get to grips with this material as soon as possible
- We will return to look at several of these topics in more detail in later lectures

SI Units

Quantity	Quantity symbol	Unit	Unit symbol
Capacitance	C	Farad	F
Charge	Q	Coulomb	C
Current	I	Ampere	A
Electromotive force	E	Volt	V
Frequency	f	Hertz	Hz
Inductance (self)	L	Henry	H
Period	T	Second	s
Potential difference	V	Volt	V
Power	P	Watt	W
Resistance	R	Ohm	Ω
Temperature	T	Kelvin	K
Time	t	Second	s

Common Prefixes

- ◆ 2^{10} (1,024) / 10^3 is kilo, denoted "K"
- ◆ 2^{20} (1,048,576) / 10^6 is mega, denoted "M"
- ◆ 2^{30} (1,073,741,824) / 10^9 is giga, denoted "G"
- ◆ 2^{40} (1,099,511,627,776) / 10^{12} is tera, denoted "T"
- ◆ 2^{50} (1,125,899,906,842,624) / 10^{15} is peta, denoted "P"
- ◆ 2^{60} (1,152,921,504,606,846,976) / 10^{18} is exa, denoted "E"
- ◆ 2^{70} (1,180,591,620,717,411,303,424) / 10^{21} is zetta, denoted "Z"
- ◆ 2^{80} (1,208,925,819,614,629,174,706,176) / 10^{24} is yotta, denoted "Y"
- ◆ 10^{-3} is milli, denoted "m"
- ◆ 10^{-6} is micro, denoted " μ "
- ◆ 10^{-9} is nano, denoted "n"
- ◆ 10^{-12} is pico, denoted "p"
- ◆ 10^{-15} is femto, denoted "f"
- ◆ 10^{-18} is atto, denoted "a"



Electrical Circuits

▣ Electric charge

- ◆ An amount of electrical particles with electrical energy
- ◆ Can be positive or negative

▣ Electric current

- ◆ A flow of electrical charge, often a flow of electrons
- ◆ Conventional current is in the opposite direction to a flow of electrons

▣ Current flow in a circuit

- ◆ A sustained current needs a complete circuit
- ◆ Also requires a stimulus to cause the charges to flow


Electromotive Force

□ Electromotive force and potential difference


- ◆ The stimulus that causes a current to flow is an **e.m.f.**
- ◆ This represents the energy introduced into the circuit by a battery or generator
- ◆ This results in an electric potential at each point in the circuit
- ◆ Between any two points in the circuit there may exist a **potential difference**
- ◆ Both e.m.f. and potential difference are measured in **volts**

A Simple Circuit Example

■ A simple circuit

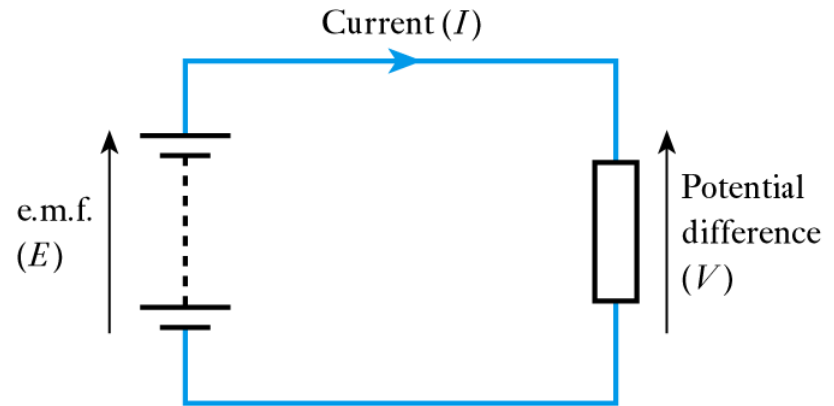


■ A water-based analogy

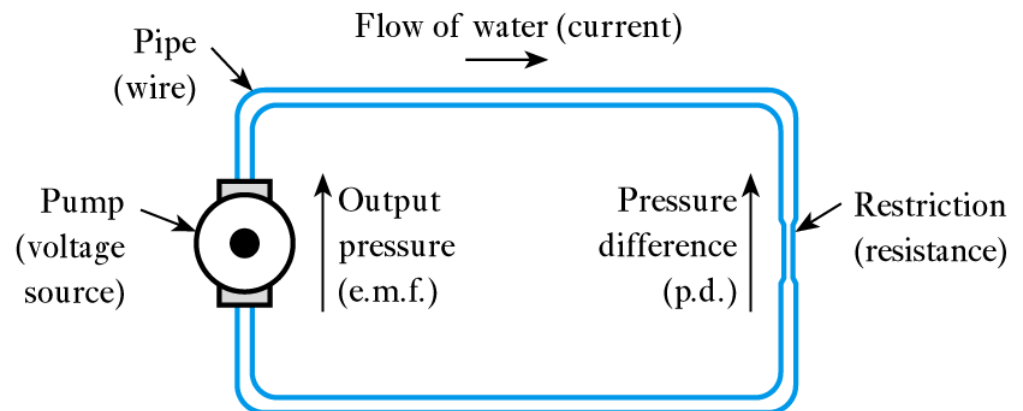


Voltage Reference Points

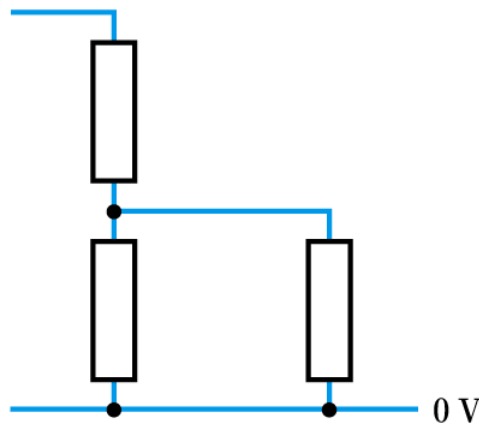- All potentials within a circuit must be measured with respect to some other point (reference point)
- We often measure voltages with respect to a zero volt reference called the **ground** or **earth**





(a)

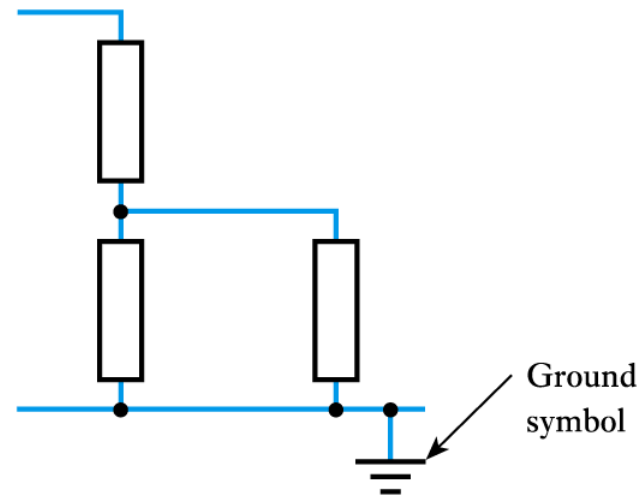

(b)

Representing Voltages

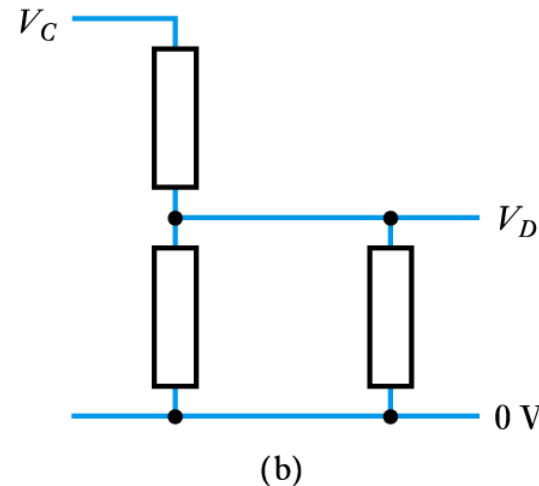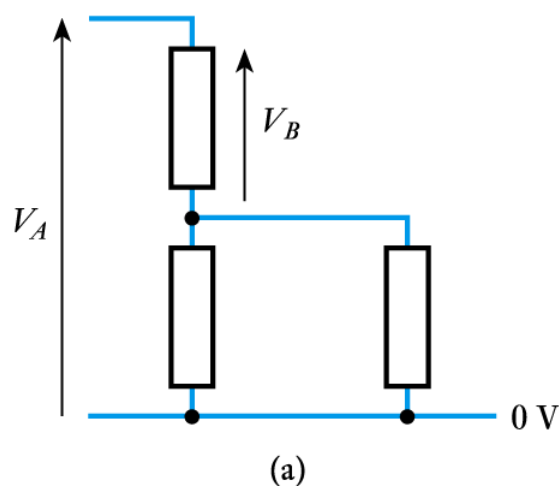- ▣ Conventions vary around the world
- ▣ We normally use an arrow, which is taken to represent the voltage on the head with respect to the tail
- ▣ Labels represent voltages with respect to earth (0V)



Direct Current and Alternating Current

- Currents in electrical circuits may be constant or may vary with time
- When currents vary with time they may be **unidirectional** or **alternating**
- When the current flowing in a conductor always flows in the same direction, this is **direct current (DC)**
- When the direction of the current periodically changes, this is **alternating current (AC)**

Resistors, Capacitors, and Inductors

■ Resistors provide resistance

- ◆ They oppose the flow of electricity
- ◆ Measured in **Ohms (Ω)**

■ Capacitors provide capacitance

- ◆ They store energy in an electric field
- ◆ Measured in **Farads (F)**


■ Inductors provide inductance

- ◆ They store energy in a magnetic field
- ◆ Measured in **Henry (H)**

■ We will look at each component in later lectures

Ohm's Law

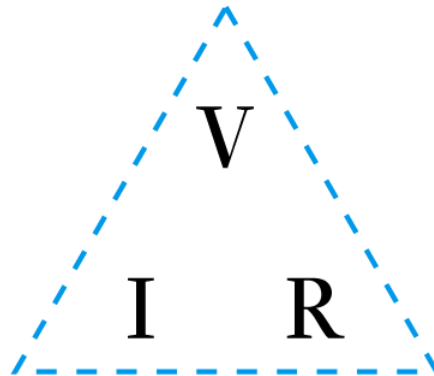- The current flowing in a conductor is directly proportional to the applied voltage V and inversely proportional to its resistance R




$$V = IR$$

$$I = V/R$$

$$R = V/I$$


Kirchhoff's Current Law (KCL)

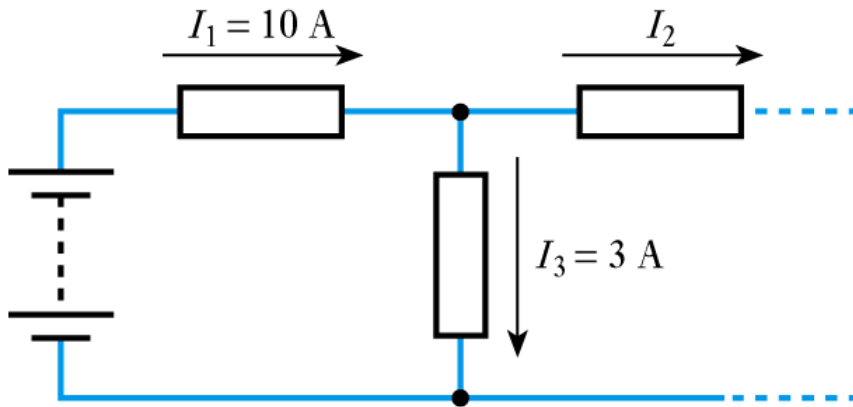- At any instant the algebraic sum of the currents flowing into any junction in a circuit is zero
- KCL example, derive I_2



Kirchhoff's Voltage Law (KVL)

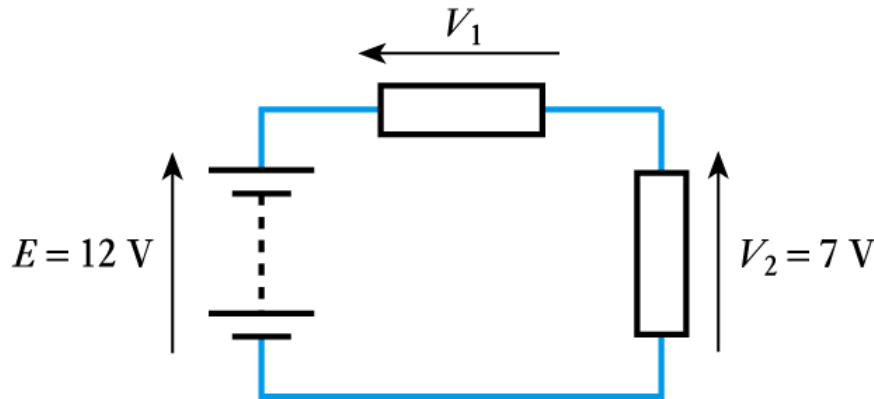- At any instant the algebraic sum of the voltages around any loop in a circuit is zero
- KVL example, derive V_1



Power Dissipation in Resistors

- The instantaneous power dissipation P of a resistor is given by the product of the voltage across it and the current passing through it. Combining this result with Ohm's law gives:

$$P = VI$$


$$P = I^2 R$$

$$P = V^2 / R$$




Resistors in Series and Parallel

■ Series

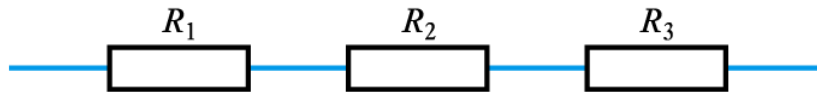

$$R = R_1 + R_2 + R_3$$


■ Parallel

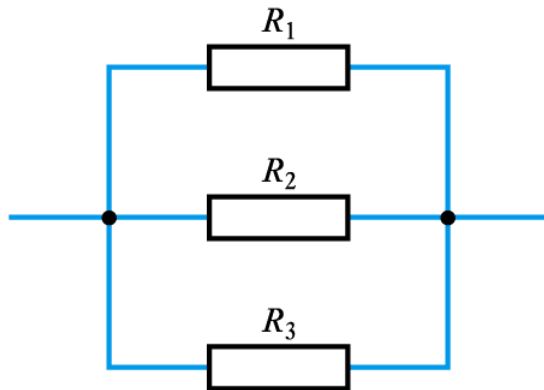

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Resistive Potential Dividers


■ General case

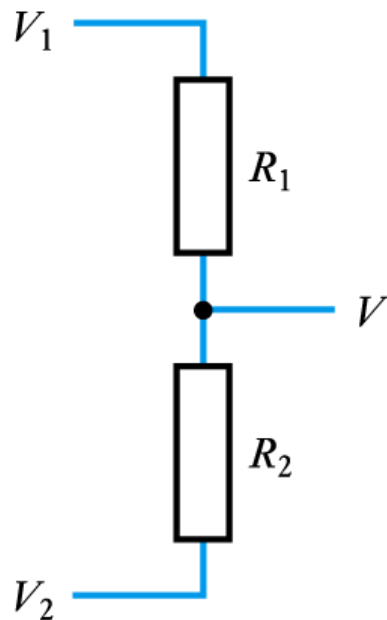

$$V = V_2 + (V_1 - V_2) \frac{R_2}{R_1 + R_2}$$


Potential Divider Example 1

Derive V

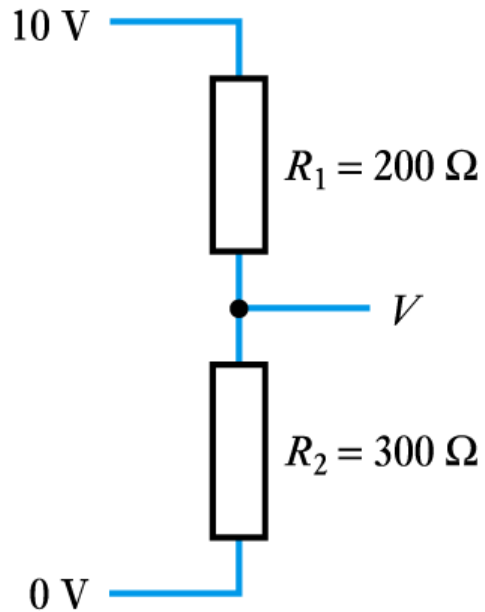


Potential Divider Example 2

▣ Derive V

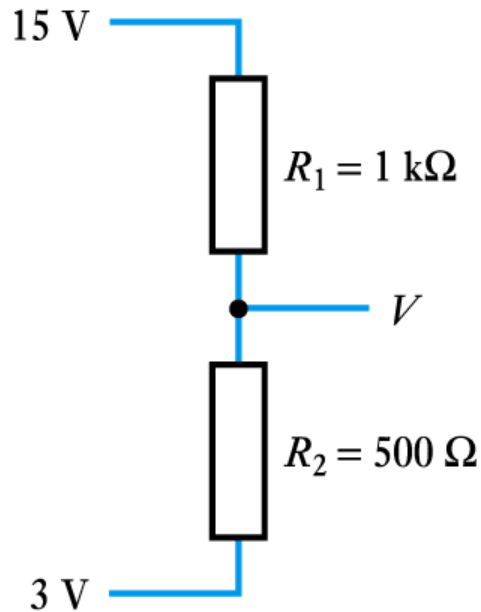

Sinusoidal Quantities

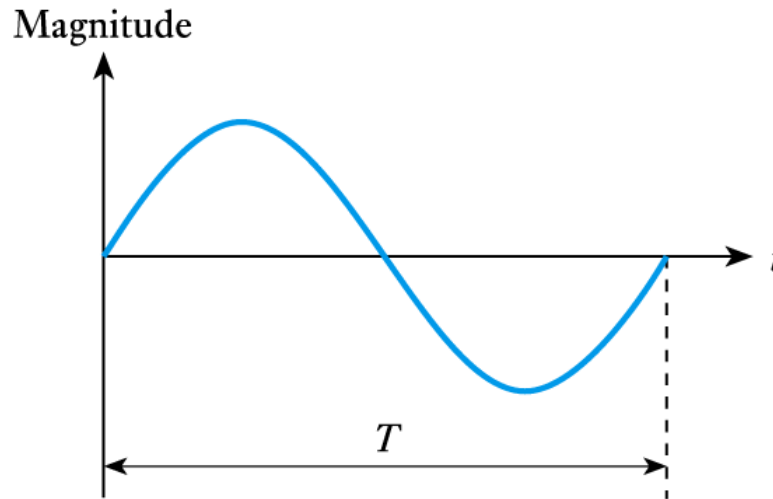- ▣ Length of time between corresponding points in successive cycles is the **period T**
- ▣ Number of cycles per second is the **frequency f**
- ▣ **$f = 1/T$**



Circuit Symbols - 1

wire (conductor)



junctions



wires crossing
(no junction)



resistor




capacitor



inductor



variable resistor

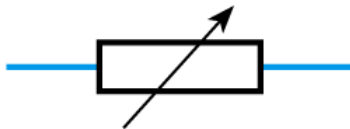

switch



lamp



American standard




IEC standard




Circuit Symbols - 2


e.m.f. (e.g. battery)

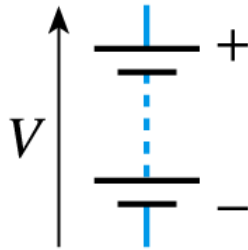

e.m.f. (e.g. battery)

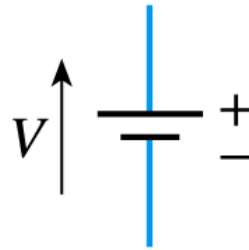

voltage source

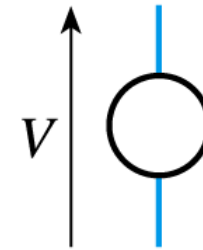

ground (zero volts)



voltmeter



ammeter



Key Points

- Understanding the next few lectures of this course relies on understanding the various topics covered in this session
- A clear understanding of the concepts of voltage and current is essential
- Ohm's Law and Kirchhoff's Laws are used extensively in later lectures
- Experience shows that students have most problems with potential dividers – a topic that is used widely in the next few lectures